

# 1. Identify Your Wires & Pins

## 1.1 GA25-370 Motor w/ Encoder

- **Thick Red** – Motor Positive
- **Thick Black** – Motor Negative
- **Thin Blue** – Encoder VCC (5 V)
- **Thin White** – Encoder GND
- **Thin Yellow** – Encoder Channel A
- **Thin Green** – Encoder Channel B

## 1.2 L298 H-Bridge Module

(As labeled on the PCB)

- **Power 1 (Vss)** – Logic supply (5 V)
  - **Power 2 (Vms)** – Motor supply (up to 12 V)
  - **Ground × 2** – All tied to common GND
  - **Enable 1&2** – PWM input for Motor A
  - **Input 1, Input 2** – Direction bits for Motor A
  - **Output 1, Output 2** – Motor A terminals
  - (The “3&4” side is unused)
- 

# 2. Prepare Your Breadboard & Power

## 1. Breadboard rails

- Tie the + **rail** to your **12 V supply** +.
- Tie the – **rail** to the supply **ground**.

## 2. Arduino power

- We'll power the L298 logic and encoder from Arduino's 5 V/ GND later.

### 3. Mount & Power the L298

3.1. Place the L298 so its pins straddle the gutter.

3.2. **Motor Supply:**

- Jumper **12 V rail** → **Power 2 (Vms)** on L298

3.3. **Logic Supply & Ground:**

- Jumper **Arduino 5 V** → **Power 1 (Vss)** on L298
- Jumper **Arduino GND** → **any L298 GND** pin
- Jumper **breadboard GND rail** → **the other L298 GND**

### 4. Wire the Motor to L298

4.1. **Motor Positive (red)** → **L298 Output 1**

4.2. **Motor Negative (black)** → **L298 Output 2**

If direction is reversed in software, swap these two.

---

### 5. Wire Control Signals (Arduino → L298)

L298 Pin	Arduino Pin	Role
<b>Enable 1&amp;2</b>	D5 (PWM)	Speed control (PWM)
<b>Input 1</b>	D2	Direction bit 1
<b>Input 2</b>	D3	Direction bit 2

- Use male-female jumpers: Arduino D2 → L298 Input1, D3 → Input2, D5 → Enable1&2.
-

## 6. Add Encoder Pull-Ups

6.1. Place **two 10 kΩ resistors** on the breadboard:

- One end of each into the **Arduino 5 V rail**.
  - The other ends reserved for Channel A & B lines.
- 

## 7. Wire the Encoder (Motor → Arduino)

Encoder Wire	Connection
<b>Blue (VCC)</b>	Arduino <b>5 V</b>
<b>White (GND)</b>	Arduino <b>GND</b> (and breadboard GND rail)
<b>Yellow (Channel A)</b>	Breadboard node → Arduino <b>D8</b> + pull-up resistor to 5 V
<b>Green (Channel B)</b>	Breadboard node → Arduino <b>D9</b> + pull-up resistor to 5 V

- At each encoder-signal node, tie the resistor's free lead to 5 V so A/B idle HIGH.
- 

## 8. Common-Ground Check

8.1. Ensure **all grounds** are tied together:

- Arduino GND
  - L298 GND pins
  - Encoder GND
  - 12 V supply ground
-

## 9. Final Inspection & Power-Up

- 9.1. Visually verify no loose or shorted wires.
  - 9.2. With a multimeter, check continuity between Arduino GND and breadboard GND.
  - 9.3. Upload your Arduino sketch.
  - 9.4. Power the 12 V supply — the motor should spin at the PWM duty you set.
  - 9.5. Open Serial Monitor at 115200 baud to see `time,voltage,RPM` streaming.
-